 


# SEMICON Solutions

---

## CMOS Logic

Trình bày: Đặng Tường Dương




# Agenda






- CMOS logic
- Logic levels
- Transmission Gates
- Sequential Logic Cells
- Datapath Logic Cells

# CMOS Logic

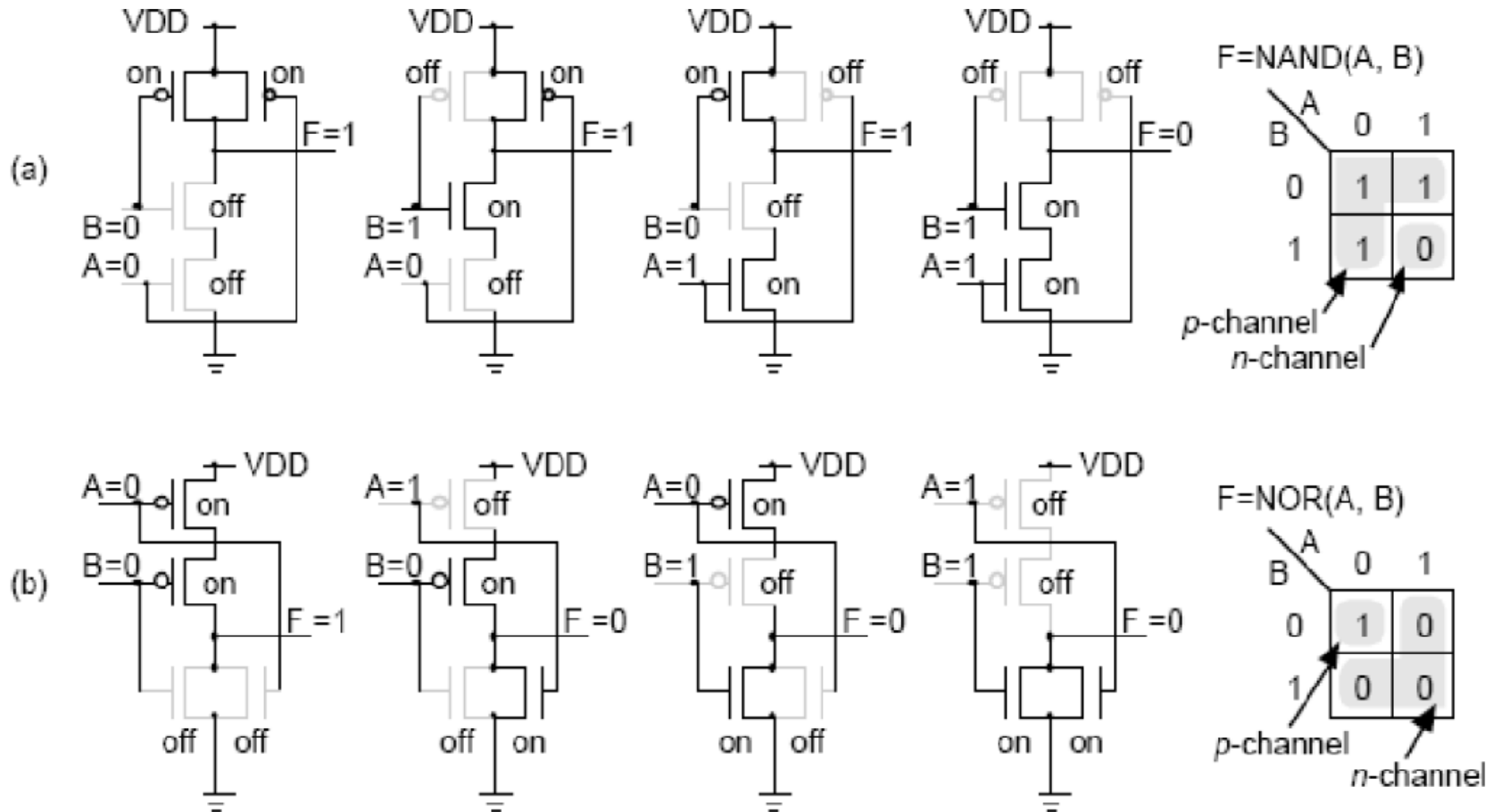


CMOS logic • a two-input **NAND gate** • a two-input **NOR gate** • **Good '1's** • **Good '0's**

# Logic Levels

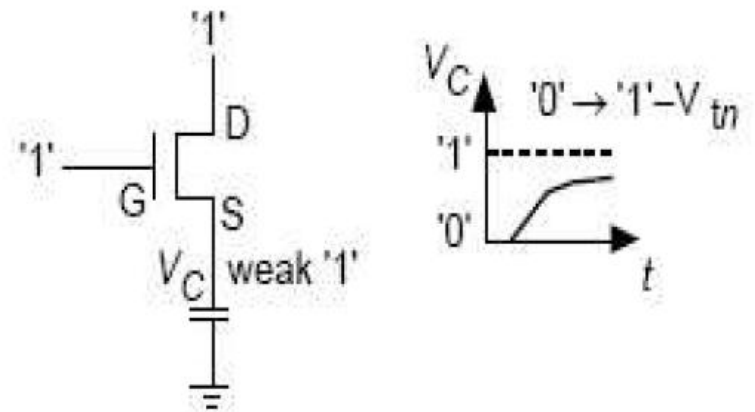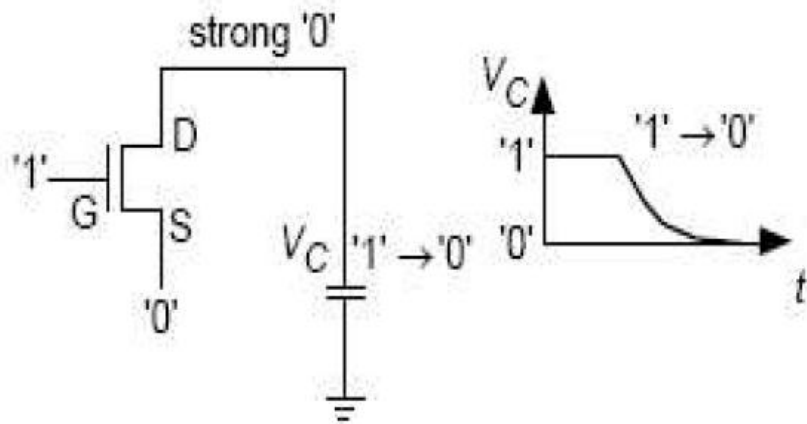 

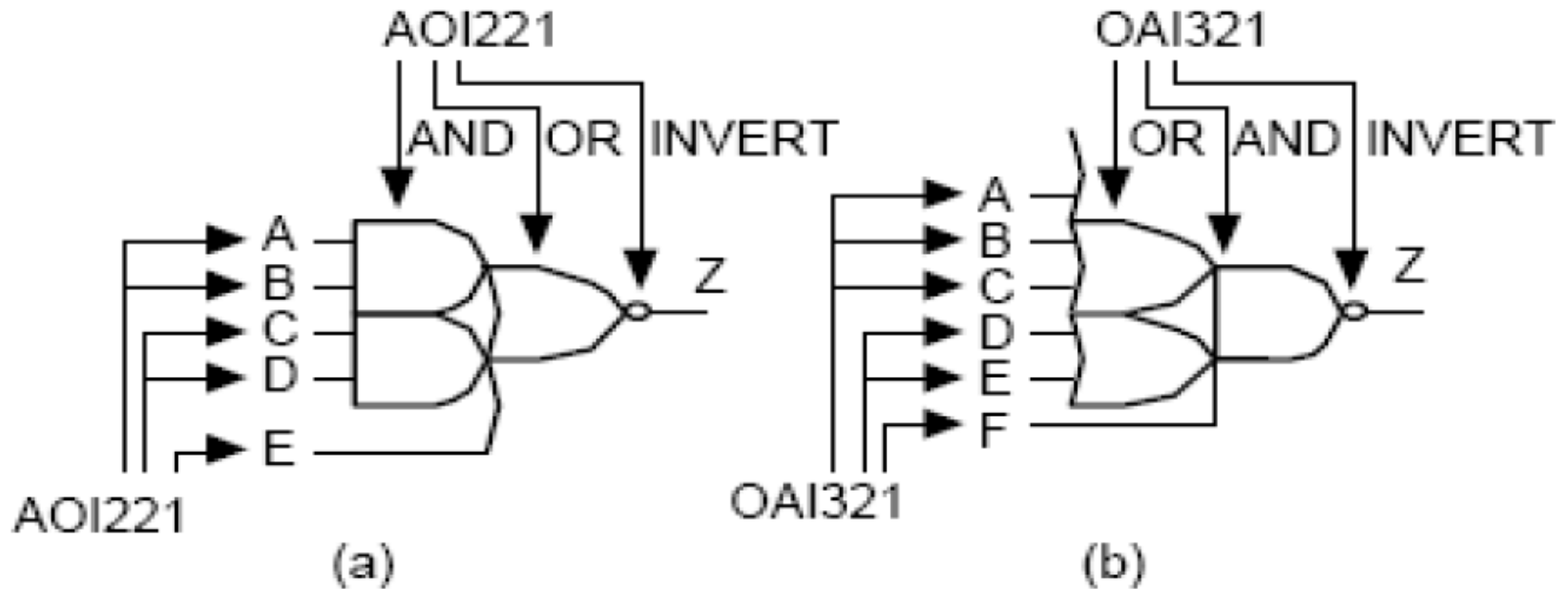
# Naming of complex CMOS combinational logic cells



## Drive Strength

We **ratio** a cell to adjust its **drive strength** and make  $b_n = b_p$  to create equal rise and fall times

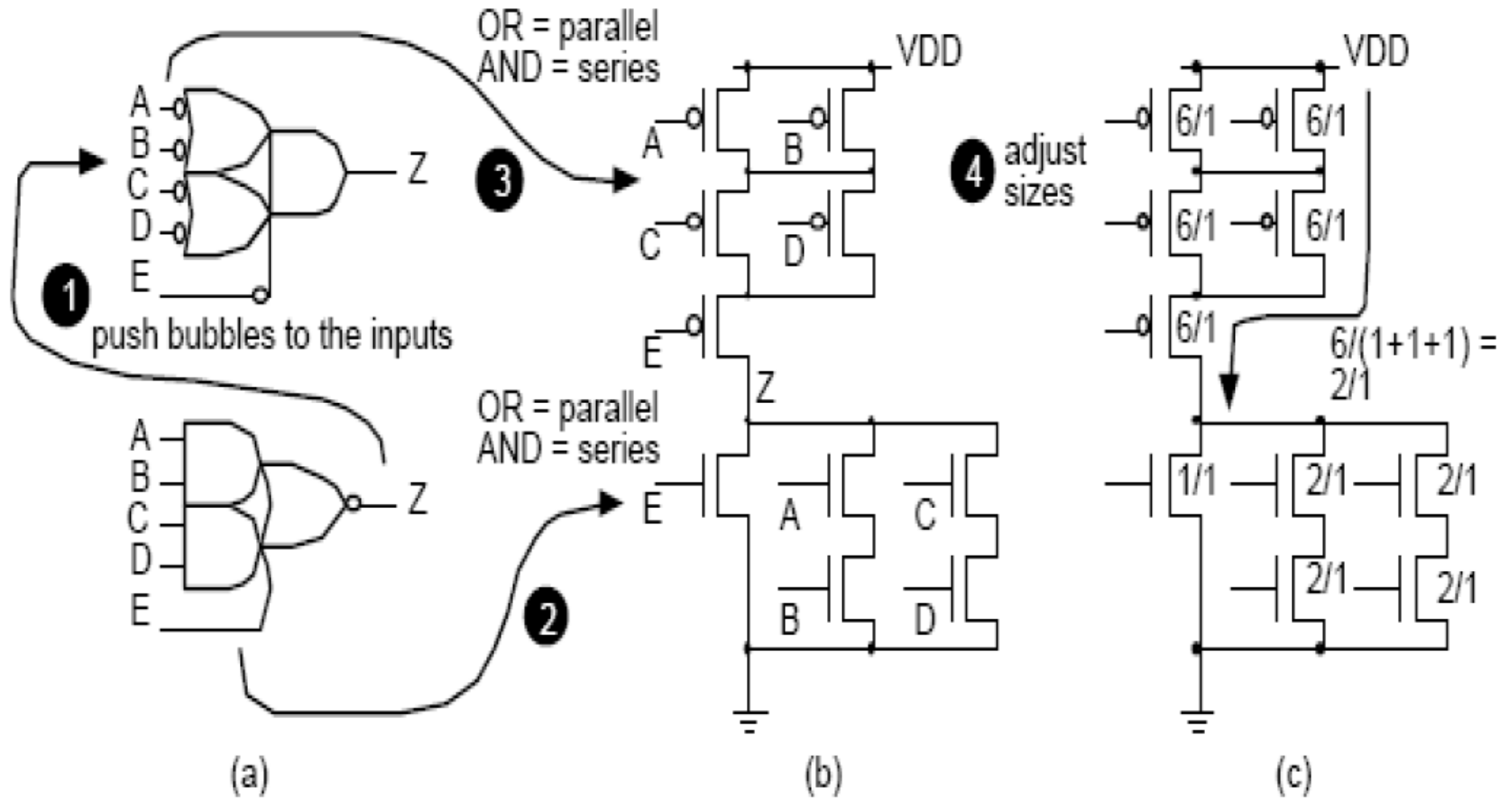
# Naming of complex CMOS combinational logic cells




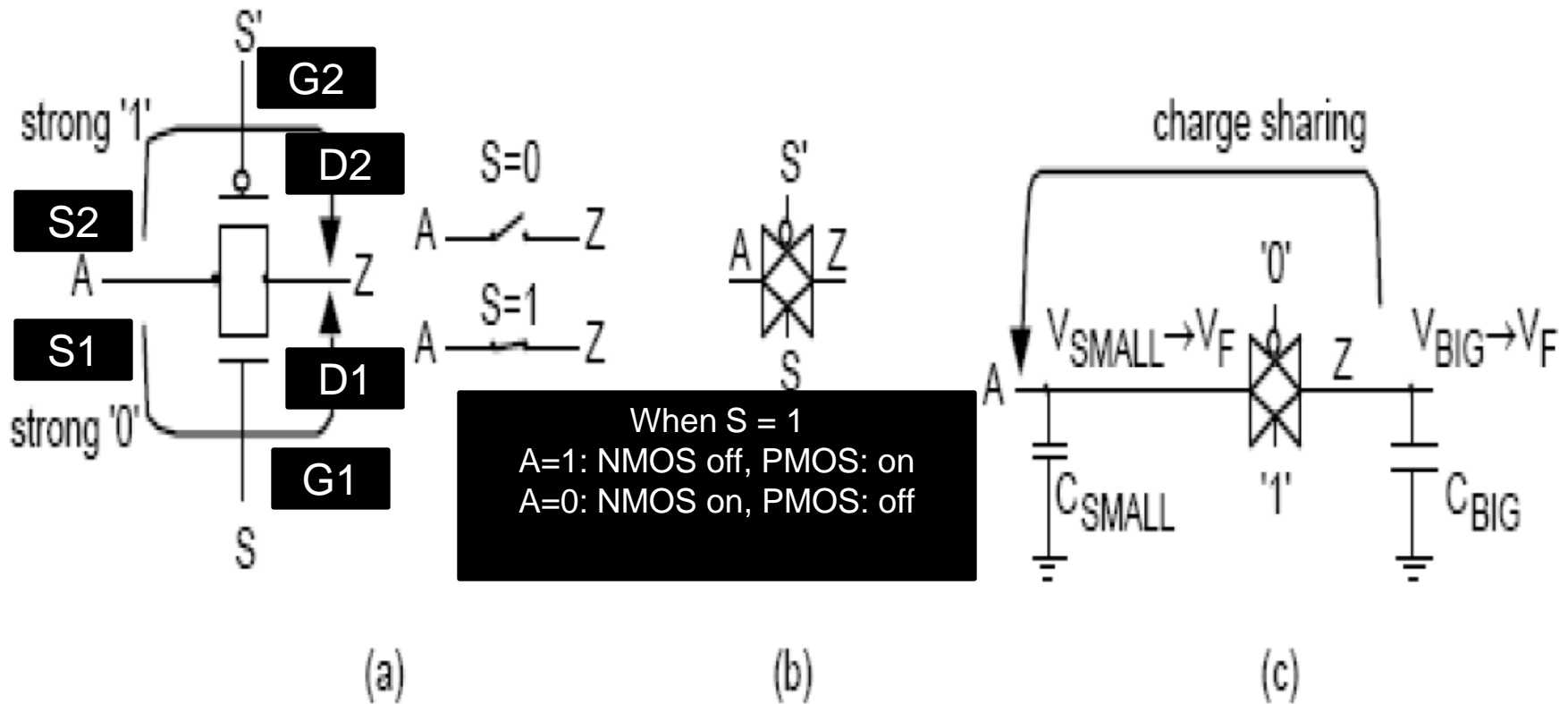
# Transmission Gates




CMOS transmission gate (TG, TX gate, pass gate, coupler)




# Sequential Logic Cells

 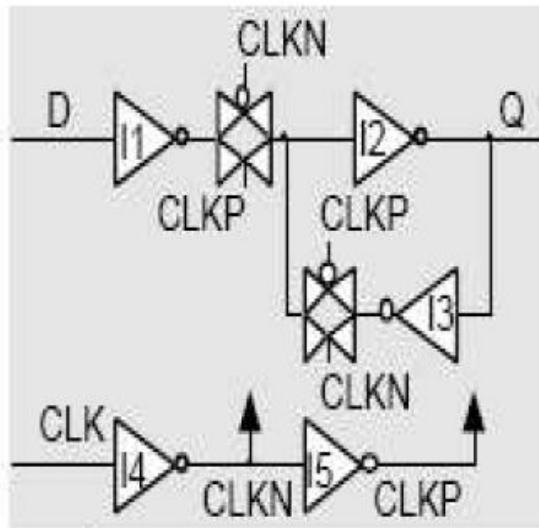

(a)

 

(b)



 


(c)


CMOS latch • enable • transparent • static • sequential logic cell • storage • initial value



# CMOS flip-flop

  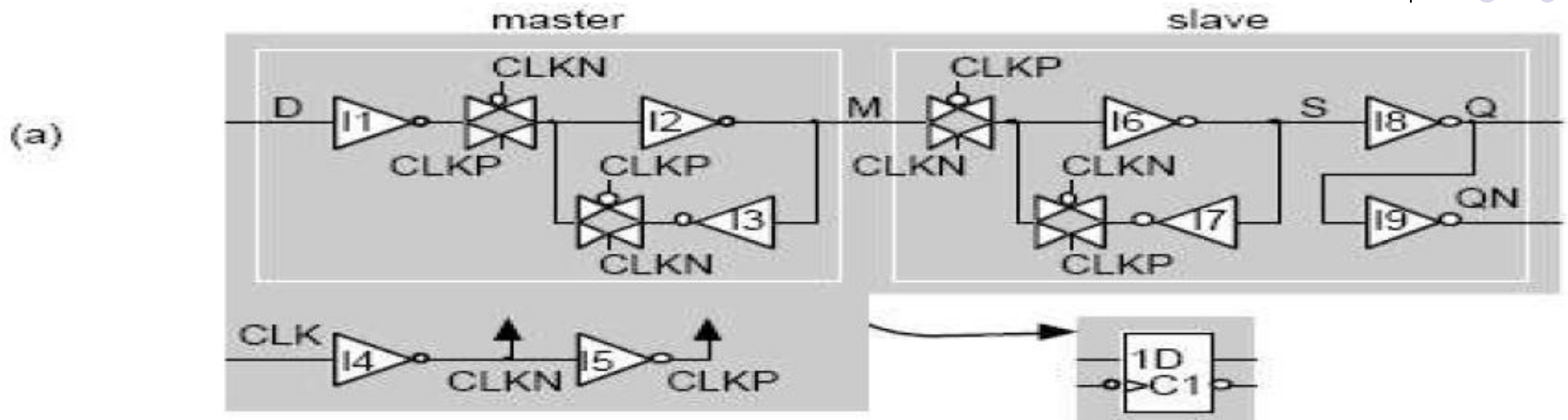


# Example of Basic Gates

 


Inverter

$$g = 1$$

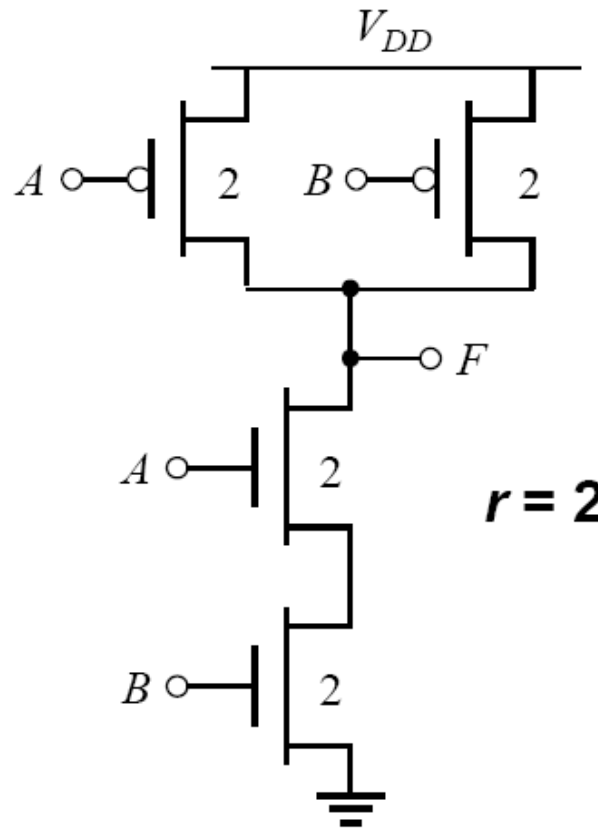

2-input NAND

$$g = 4/3$$

 

2-input NOR

$$g = 5/3$$



# Câu Hỏi & Trả Lời